

Lecture 12: Circuits for CSS codes

12.1 Coupling the error syndrome

$$C_2^\perp \leq C_1 = [n, k_1, d_1] \quad C_1^\perp \leq C_2 = [n, k_2, d_2]$$


$$G_1 = \left[\underbrace{\begin{matrix} H_2 \\ D_1 \end{matrix}}_n \right]^{n-k_2} \Bigg\}^{k_1} \quad G_2 = \left[\underbrace{\begin{matrix} H_1 \\ D_2 \end{matrix}}_n \right]^{n-k_1} \Bigg\}^{k_2}$$

Syndrome for bit-flip (D_x) errors:


$$S_x: \underbrace{|x\rangle}_n \underbrace{|y\rangle}_{n-k_1} \mapsto |x\rangle |x \cdot H_1^t + y\rangle$$

CNOT: $\begin{matrix} |x\rangle \\ |y\rangle \end{matrix} \xrightarrow{\text{CNOT}} \begin{matrix} |x\rangle \\ |x+y\rangle \end{matrix} \quad \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$
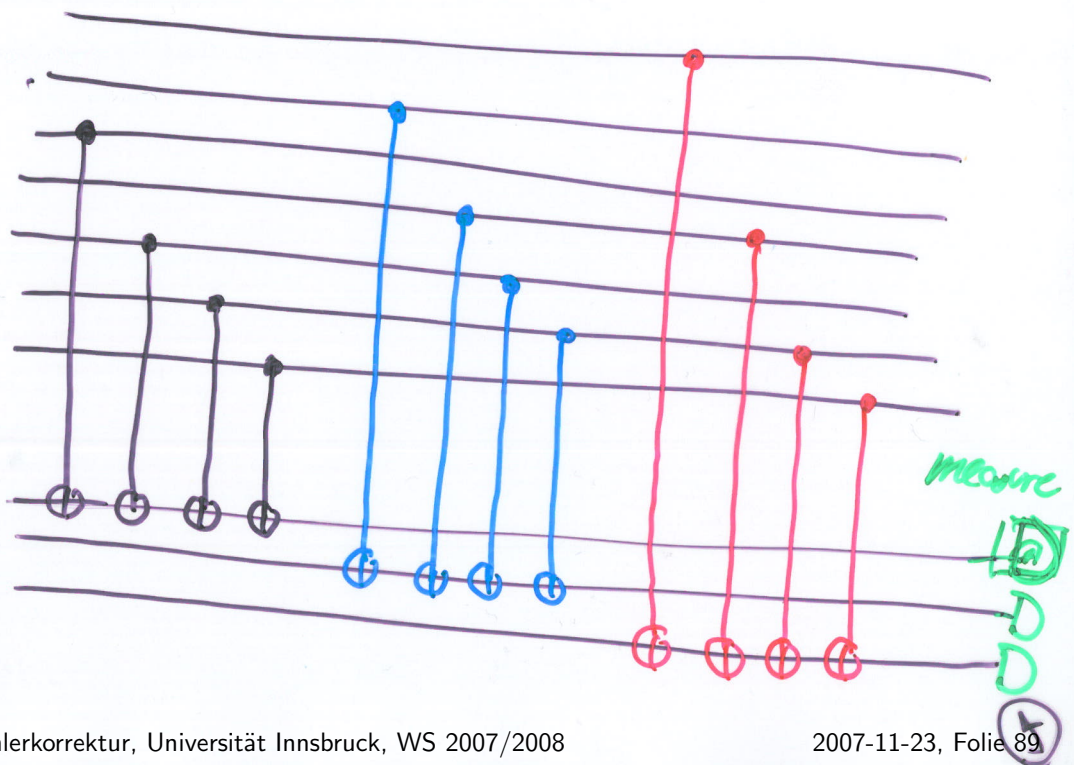
$$H_1^t = \begin{pmatrix} 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \\ 1 & 1 & 0 & 0 \\ 1 & 1 & 1 & 1 \\ 1 & 0 & 1 & 1 \end{pmatrix} \begin{matrix} 7 \\ 7 \\ 6 \\ 6 \\ 3 \end{matrix}$$




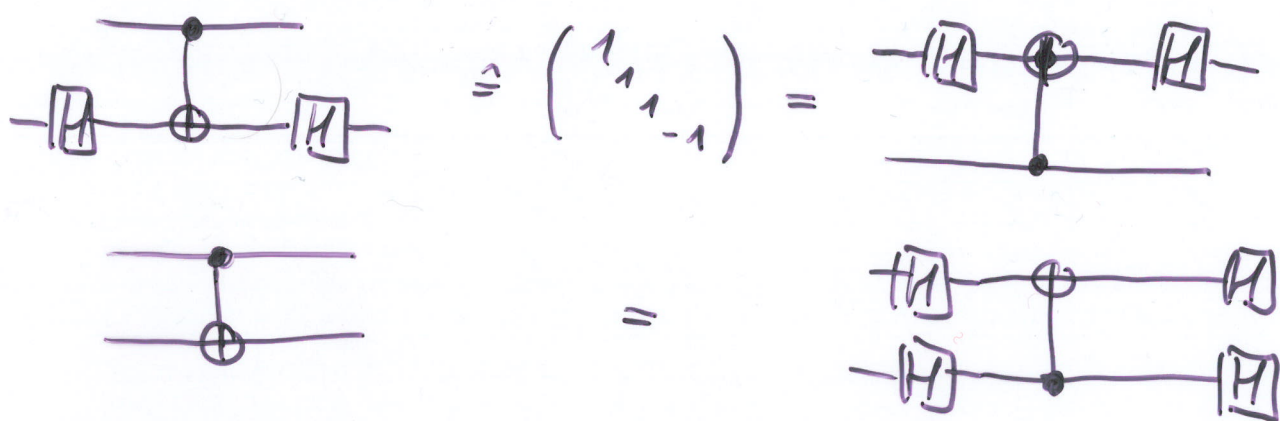problem: This way of compiling an error syndrome is not fault tolerant, as many control qubits are coupled to the same target qubit $\Rightarrow$ single errors may spread over many locations




error propagation for CNOT:

X:

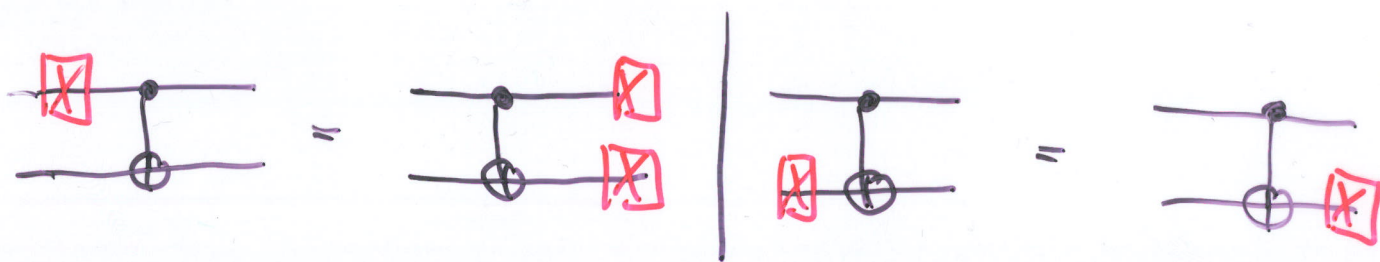


Z:

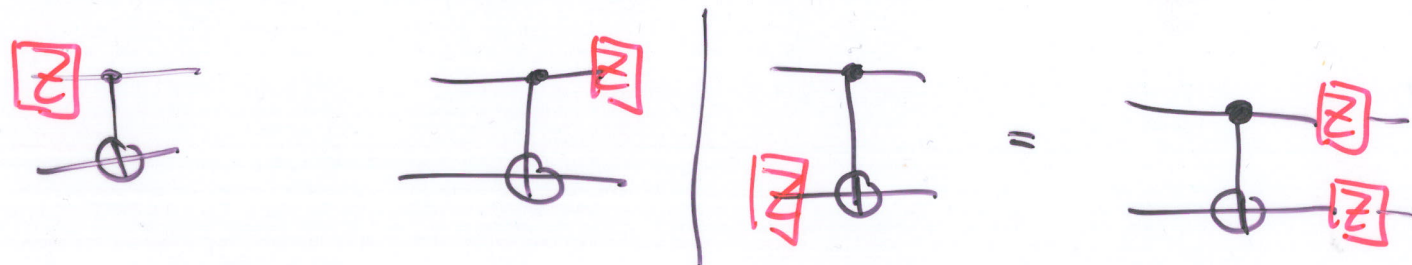

X propagates from control to target
Z propagates from target to control

12.2 Fault tolerant synchronous computation

3

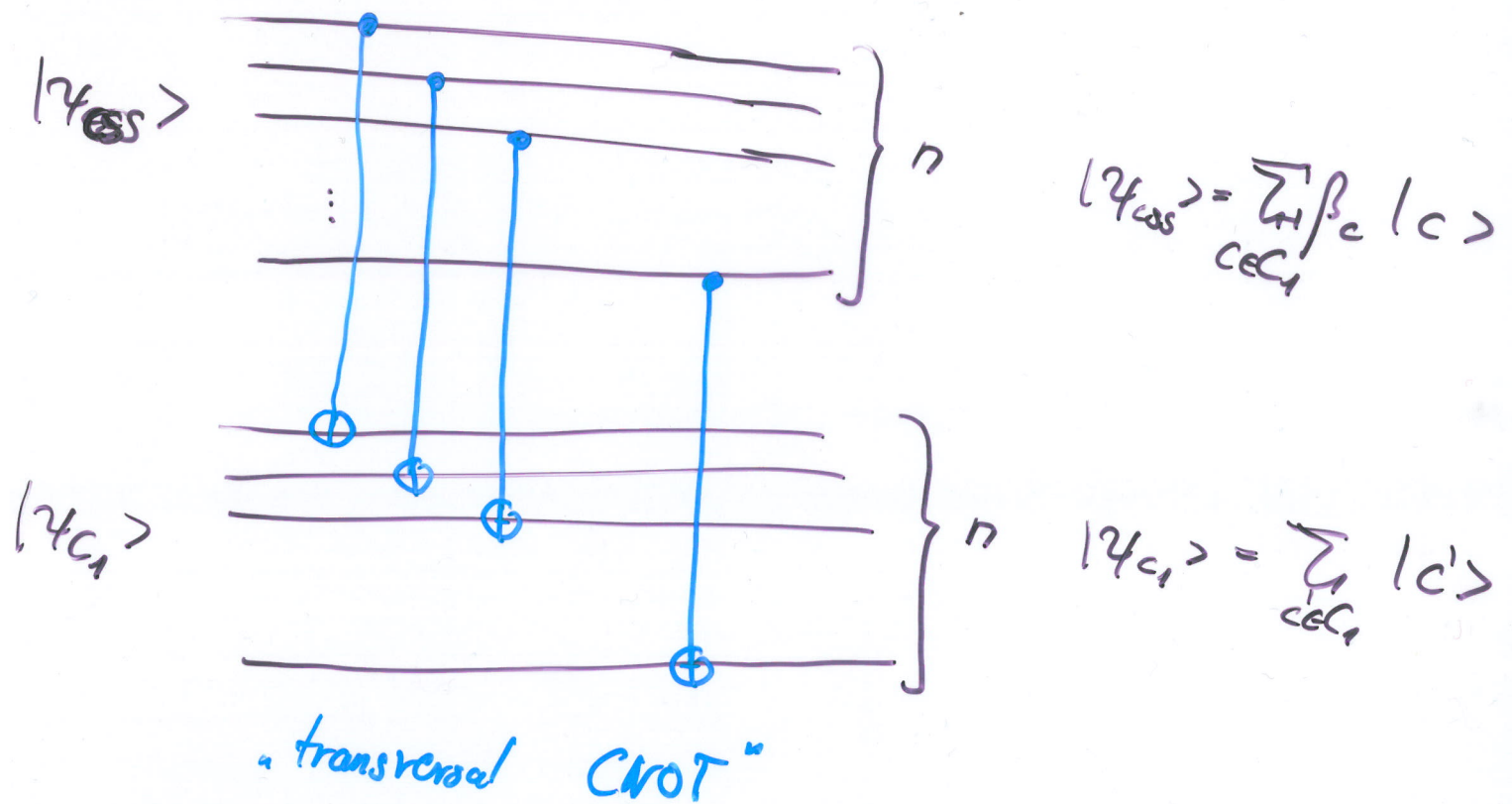

$$(CNOT^{\otimes n}) |\psi_{\text{css}}\rangle |\psi_{C_1}\rangle$$

$$= \sum_{e_x} \sum_{c \in C_1} \beta_c |c + e_x\rangle \sum_{c' \in C_1} |c + c' + e_x\rangle$$

↓ measurement

random codeword $\tilde{c} \in C_1$

or $\tilde{c} + \tilde{e}_x$

then compute $(\tilde{c} + \tilde{e}_x) \cdot H_1^t = \tilde{e}_x \cdot H_1^t$
on a classical computer